

EELE 250: Circuits, Devices, and Motors

Lecture 6

Assignment Reminder

- Read 3.1 - 3.3
- Practice problems:
 - **T2.2, T2.4, T2.5**
 - **P3.6, P3.9, P3.24**
- D2L Quiz #3 *by 11AM* on Monday 16 Sept.

Exam Reminder

- **Exam #1 in class on Wednesday 18 Sept.**
- **Covers material from chapters 1 and 2.**
- **Closed book. One 8.5"x11" sheet of handwritten notes. Pencil. Calculator.**
- **Format: Mix of multiple choice and short answer questions.**
- **Special review/problem session: Thursday, Sept. 12, 4:00PM, Cobleigh 608**

Circuit Analysis: review

- General techniques to find currents and voltages in electrical networks
- Use KVL, KCL, and Ohm's Law
- Remember: voltages and currents can be positive or negative, so be meticulous with the math!

A question...

- What is your instructor's name?
 - A. Prof. Mayer
 - B. Prof. Mahar
 - C. Prof. Meagher
 - D. Prof. Mahr
 - E. Prof. Maher


Equivalent Circuits

- We often want to connect one circuit to another. The *output* of one circuit connects to the *input* of another circuit.
 - *Think of some examples of an electrical output connected to an electrical input...*
- We can characterize a complicated linear circuit by determining a simpler circuit that behaves the same way (as was done for parallel and series resistor circuits).

Equivalent Circuits (cont.)


- A “two-terminal circuit” means a circuit with two nodes available externally.
- Sometimes this is an electrical *input* or an *output*: one node is ground and the other node is a signal voltage with respect to ground.
- If the circuit attached to the two terminals contains only linear elements, there exists an equivalent circuit containing just a single voltage source and a single series resistance.

Thévenin Equivalent

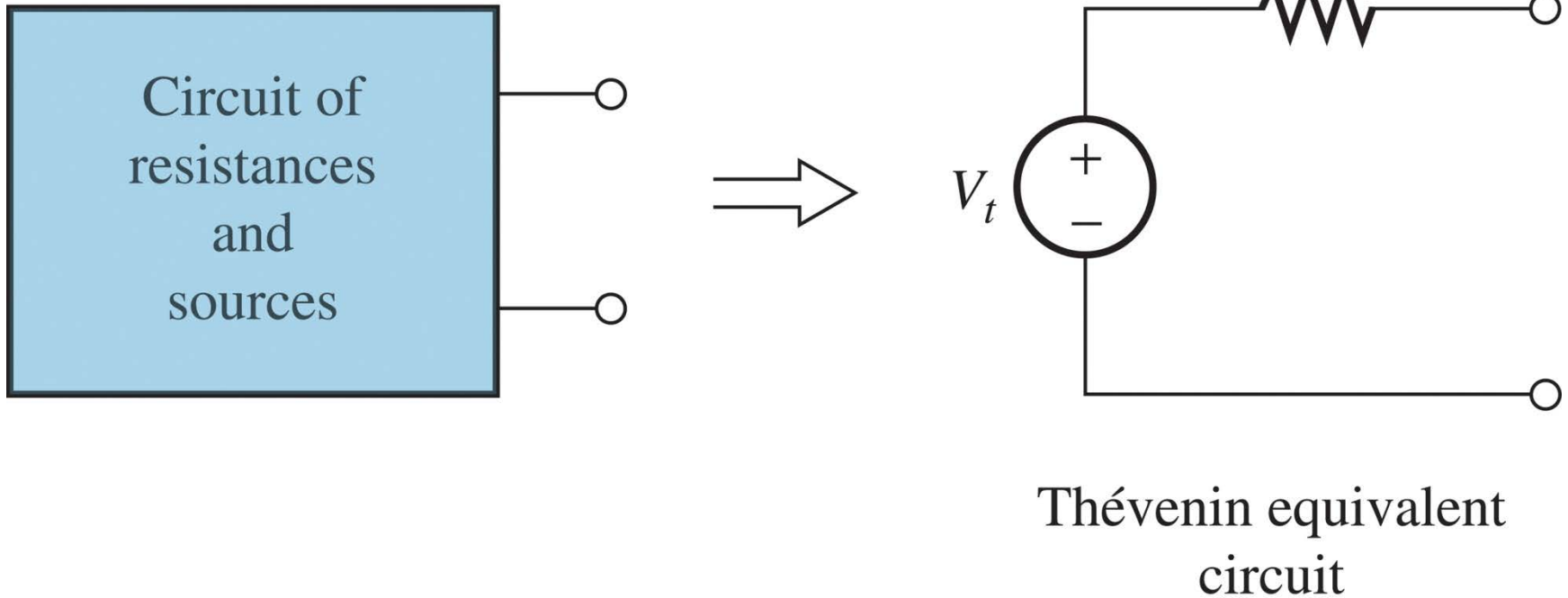


Thévenin Equivalent (cont.)

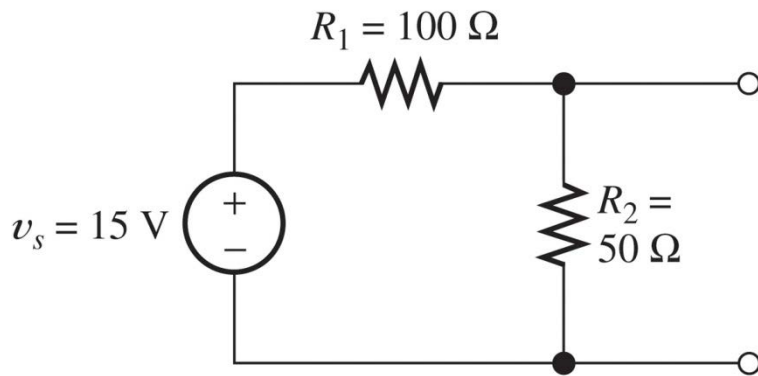- V_t is the *open circuit voltage* between the two terminals
- R_t is the ratio of V_t divided by the *short circuit current* (I_{sc}) between the two terminals




(a) Original circuit

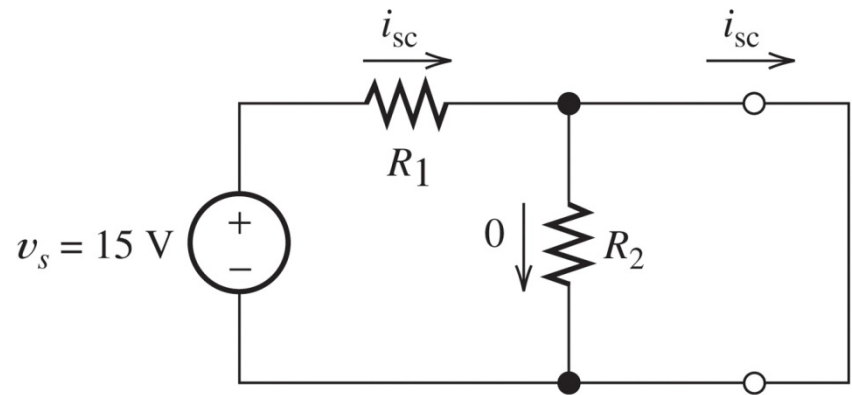

(c) Analysis with a short circuit

Thévenin Equivalent (cont.)

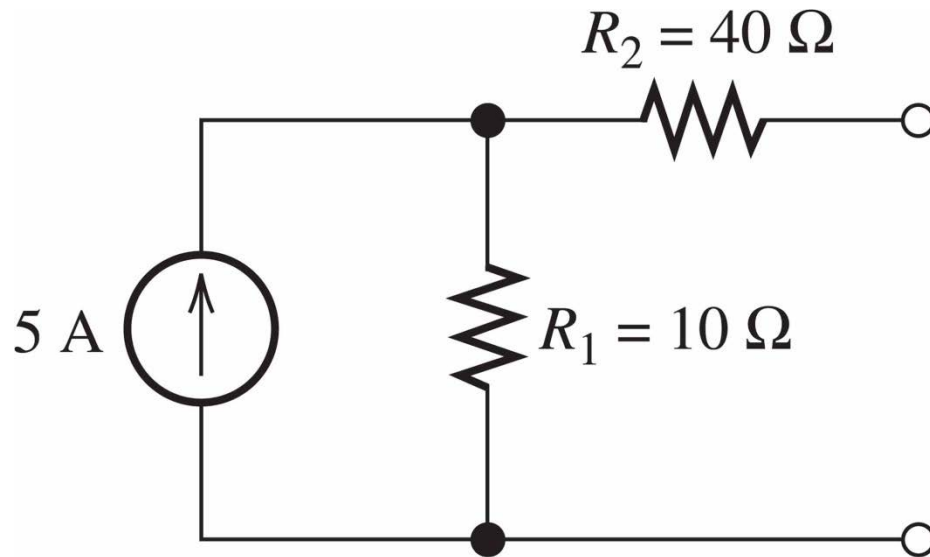

What is V_{OC} ?


- (a) 5 volts (b) 50 volts (c) 100 volts (d) 150 volts (e) 200 volts

What is I_{SC} ?

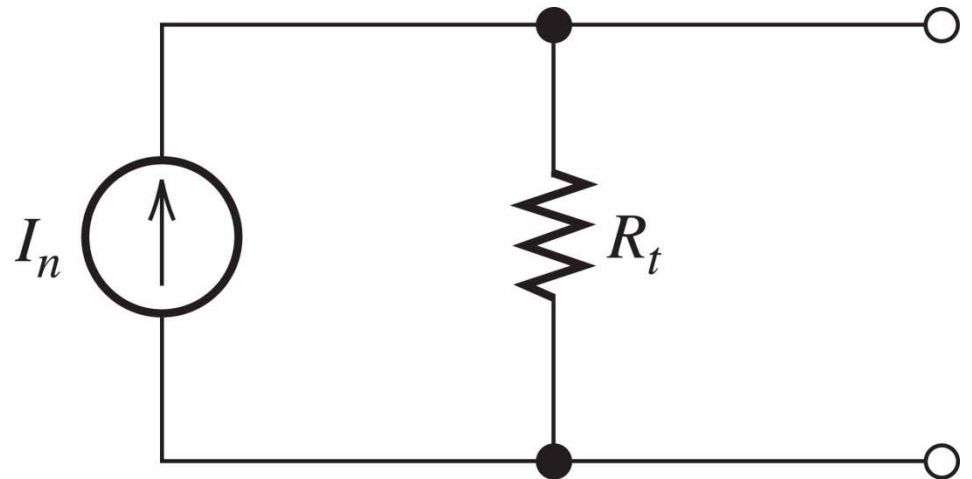- (a) 1 amp (b) 2 amps (c) 3 amps (d) 4 amps (e) 5 amps

Norton Equivalent


- Another formulation that is equivalent to the Thévenin representation includes a current source and a parallel resistance.
- $I_{\text{norton}} = I_{\text{SC}}$
- $R_t = R_{\text{norton}} = V_{\text{OC}}/I_{\text{SC}}$
- $V_{\text{OC}} = I_{\text{norton}} * R_t$




Finding R_t

- It is possible to find R_t by *turning off* the independent voltage and current sources in the circuit and simplifying the resistive network
 - Turn off voltage source: set voltage to zero, which is a short circuit
 - Turn off current source: set current to zero, which is an open circuit

Finding R_t (cont.)

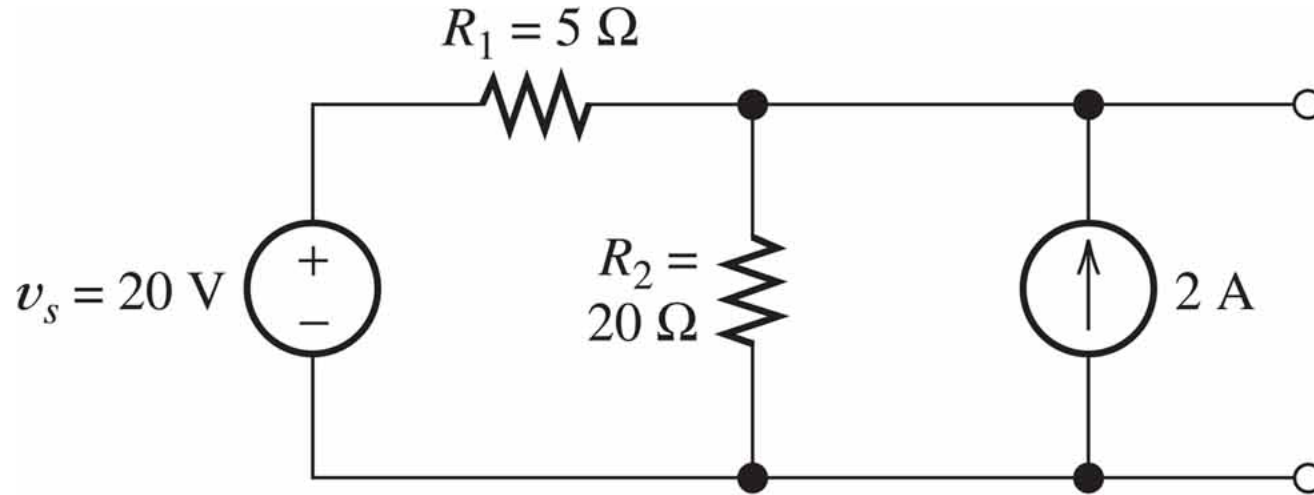


(a) Original circuit

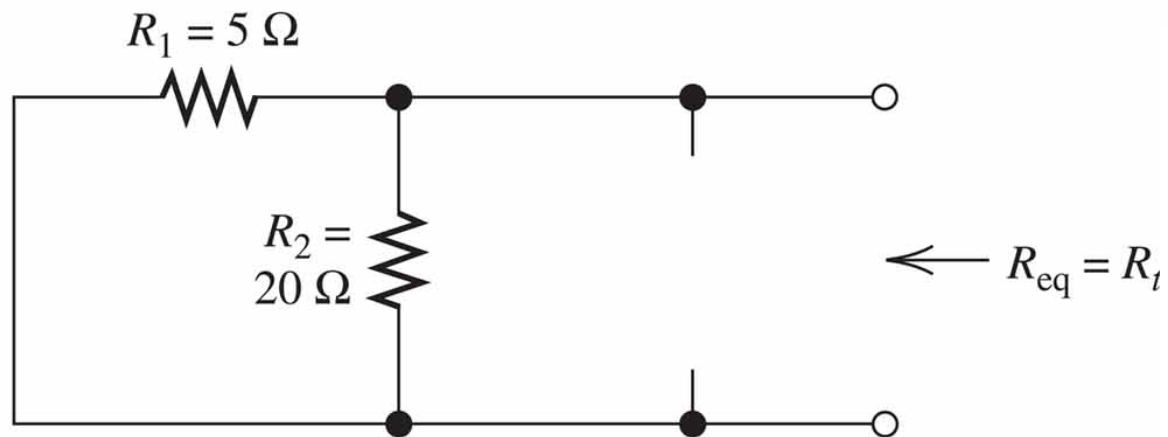

(b) Circuit with sources zeroed

Simplifying via Source Transformation

- Thévenin and Norton transformation

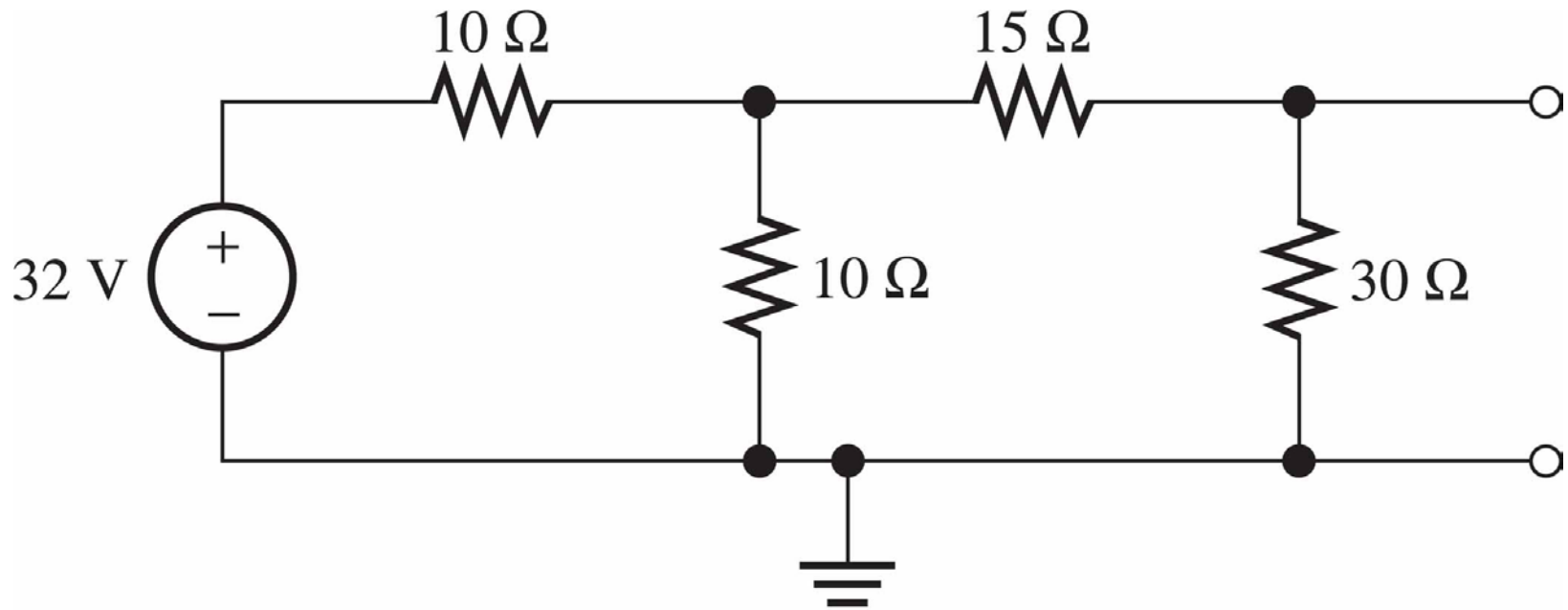

Summary and Review

- Source transformation by equivalent Thévenin and Norton circuits
- Use open circuit voltage and short-circuit current at the terminals
- $V_{\text{thevenin}} = V_{\text{oc}}$
- $I_{\text{norton}} = I_{\text{sc}}$
- $R_t = V_{\text{oc}}/I_{\text{sc}}$