

EELE 250: Circuits, Devices, and Motors

Lecture 10

Assignment Reminder


- Read 4.1 - 4.3 AND 5.1 - 5.4
- Practice Problems:
 - P3.60, 3.64, 3.72
 - P4.3, 4.8, 4.9, 4.23, 4.37, 4.38
- D2L Quiz #4 is due by 11AM on Wednesday, Sept. 25. Quiz #5 will be posted on Wednesday, and it is due by 11AM on Monday, Sept. 30.

Transients with C and L

- Transient analysis: it takes time to change voltage on a capacitor or change current in an inductor
 - Analysis uses node voltage or mesh current analysis
 - Typically need to consider the circuit just before $t=0$ ($t<0$) and after $t=0$ ($t=0+$)
- Cannot instantly change inductor current
 - Cannot instantly change capacitor voltage

Discharging a capacitor

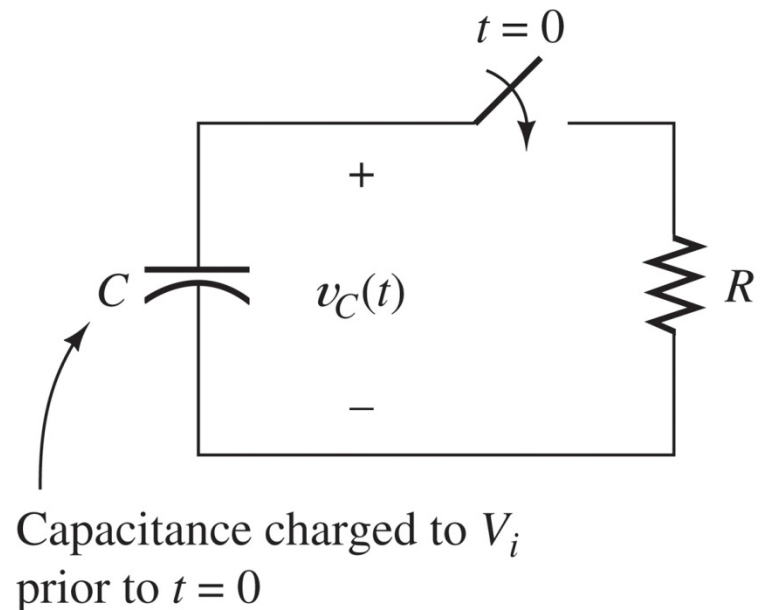- Consider a capacitor, C , charged to some initial voltage, v_i
- At $t=0$, a resistance R is connected across the capacitor: current will start to flow, because V_i across R (Ohm's Law).



Discharge current

- Current in capacitor: $-C \frac{dv}{dt}$
- Current in resistor: v/R
- Node equation: $C \frac{dv}{dt} + \frac{v}{R} = 0$
- Or in standard form: $\frac{dv_c(t)}{dt} + \left(\frac{1}{RC}\right) v_c(t) = 0$

Discharge current (cont.)

$$\frac{dv_c(t)}{dt} + \left(\frac{1}{RC}\right)v_c(t) = 0$$

- Solution of differential equation is an exponential: $v_c(t) = Ke^{st}$

$$\text{So } sKe^{st} + \left(\frac{1}{RC}\right)Ke^{st} = 0$$

- Using initial conditions: $v_c(0) = V_i$

$$s = -\frac{1}{RC} \quad \text{and} \quad K = V_i$$

Discharge Current (cont.)

- In exponent, $s \cdot t$ must be dimensionless, so $s = -\frac{1}{RC}$ implies RC has units of *seconds*.
- RC is called the *time constant*.
- The bigger the RC time constant, the slower the discharge time

Charging a capacitor

- Node equation for RC switched in series with voltage source:

- $$C \frac{dv_c(t)}{dt} + \frac{v_c(t) - V_s}{R} = 0$$
$$v_c(t) = K_1 + K_2 e^{st}$$

- General solution:

$$v_c(t) = v_\infty + (v_0 - v_\infty) e^{-t/RC}$$

$$\tau = \text{time constant} = RC$$

Inductor transient analysis

- Procedure similar to capacitor analysis, except with differential equation involving inductor voltage in terms of inductor current
- General solution:

$$i_L(t) = i_\infty + (i_0 - i_\infty)e^{-t/(L/R)}$$

$$\tau = \text{time constant} = \frac{L}{R}$$

General Procedure for RL and RC

- Identify initial conditions:
 i_0 in inductor; v_0 for capacitor
- Identify final conditions:
 i_∞ for inductor; v_∞ for capacitor
- Identify equivalent resistance (Thevenin)
“seen” by inductor or capacitor.
- Compute time constant:
 L/R_{eq} for inductor; $R_{eq} \cdot C$ for capacitor
- Then apply to general equation!

Summary and Review

- Capacitor and inductor transient analysis uses the same KVL and KCL principles we learned in Chapter 2, except with $C \, dv/dt$ and $L \, di/dt$ included along with Ohm's Law.
- Standard solution form: $K_1 + K_2 e^{st}$

- General solutions:

$$v_c(t) = v_\infty + (v_0 - v_\infty)e^{-t/RC}$$

$$i_L(t) = i_\infty + (i_0 - i_\infty)e^{-t/(L/R)}$$