

# EELE 250: Circuits, Devices, and Motors

Lecture 10

# Assignment Reminder


- Read 4.1 - 4.3 AND 5.1 – 5.4
- Practice problems:
  - P3.46, P3.54, P3.62, P3.63
  - P4.3, P4.5, P4.33, P4.39
- D2L Quiz #5 by 11AM on Monday 3 Oct.
- REMINDER: Work on your Lab #3 formal report. The reports are due at lab time during the week of Oct. 3.

# Transients with C and L

- Transient analysis: it takes time to change voltage on a capacitor or change current in an inductor
  - Analysis uses node voltage or mesh current analysis
  - Typically need to consider the circuit just before  $t=0$  ( $t<0$ ) and after  $t=0$  ( $t=0+$ )
- Cannot instantly change inductor current
  - Cannot instantly change capacitor voltage
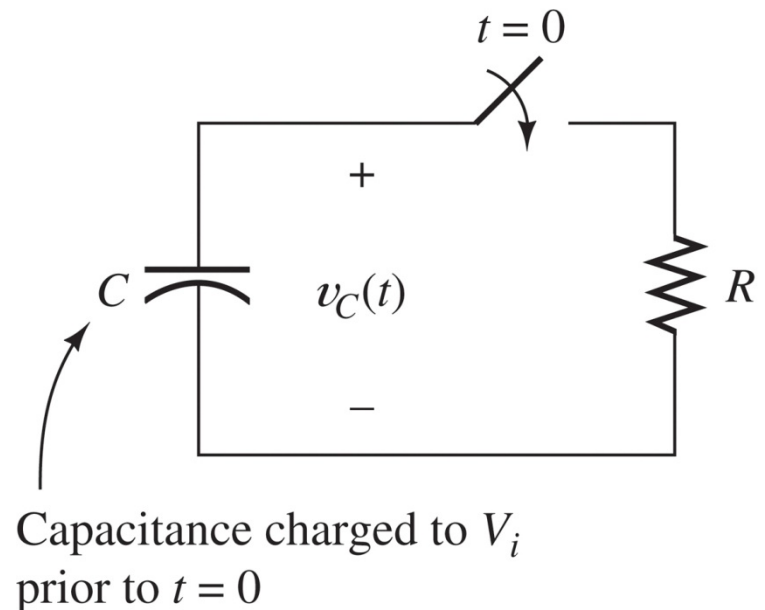
# Discharging a capacitor

- Consider a capacitor,  $C$ , charged to some initial voltage,  $v_i$
- At  $t=0$ , a resistance  $R$  is connected across the capacitor: current will start to flow, because  $V_i$  across  $R$  (Ohm's Law).



# Discharge current

- Current in capacitor:  $-C \frac{dv}{dt}$
- Current in resistor:  $v/R$
- Node equation:  $C \frac{dv}{dt} + \frac{v}{R} = 0$
- Or in standard form:  $\frac{dv_c(t)}{dt} + \left(\frac{1}{RC}\right) v_c(t) = 0$

# Discharge current (cont.)

$$\frac{dv_c(t)}{dt} + \left(\frac{1}{RC}\right)v_c(t) = 0$$

- Solution of differential equation is an exponential:  $v_c(t) = Ke^{st}$

$$\text{So } sKe^{st} + \left(\frac{1}{RC}\right)Ke^{st} = 0$$

- Using initial conditions:  $v_c(0) = V_i$

$$s = -\frac{1}{RC} \quad \text{and} \quad K = V_i$$

# Discharge Current (cont.)

- In exponent,  $s \cdot t$  must be dimensionless, so  $s = -\frac{1}{RC}$  implies  $RC$  has units of *seconds*.
- $RC$  is called the *time constant*.
- The bigger the  $RC$  time constant, the slower the discharge time

# Charging a capacitor

- Node equation for  $RC$  switched in series with voltage source:

- $$C \frac{dv_c(t)}{dt} + \frac{v_c(t) - V_s}{R} = 0$$
$$v_c(t) = K_1 + K_2 e^{st}$$

- General solution:

$$v_c(t) = v_\infty + (v_0 - v_\infty) e^{-t/RC}$$

$$\tau = \text{time constant} = RC$$



# Inductor transient analysis

- Procedure similar to capacitor analysis, except with differential equation involving inductor voltage in terms of inductor current
- General solution:

$$i_L(t) = i_\infty + (i_0 - i_\infty)e^{-t/(L/R)}$$

$$\tau = \text{time constant} = \frac{L}{R}$$

# General Procedure for RL and RC

- Identify initial conditions:  
 $i_0$  in inductor;  $v_0$  for capacitor
- Identify final conditions:  
 $i_\infty$  for inductor;  $v_\infty$  for capacitor
- Identify equivalent resistance (Thevenin)  
“seen” by inductor or capacitor.
- Compute time constant:  
 $L/R_{eq}$  for inductor;  $R_{eq} \cdot C$  for capacitor
- Then apply to general equation!

# Summary and Review

- Capacitor and inductor transient analysis uses the same KVL and KCL principles we learned in Chapter 2, except with  $C \, dv/dt$  and  $L \, di/dt$  included along with Ohm's Law.
- Standard solution form:  $K_1 + K_2 e^{st}$

- General solutions:

$$v_c(t) = v_\infty + (v_0 - v_\infty)e^{-t/RC}$$

$$i_L(t) = i_\infty + (i_0 - i_\infty)e^{-t/(L/R)}$$