

***P5.23.** Reduce $5 \cos(\omega t + 75^\circ) - 3 \cos(\omega t - 75^\circ) + 4 \sin(\omega t)$ to the form $V_m \cos(\omega t + \theta)$.

P5.23* We are given the expression

$$5 \cos(\omega t + 75^\circ) - 3 \cos(\omega t - 75^\circ) + 4 \sin(\omega t)$$

Converting to phasors we obtain

$$\begin{aligned} 5\angle 75^\circ - 3\angle -75^\circ + 4\angle -90^\circ &= \\ 1.2941 + j4.8296 - (0.7765 - j2.8978) - j4 &= \\ 0.5176 + j3.7274 &= 3.763\angle 82.09^\circ \end{aligned}$$

Thus, we have

$$\begin{aligned} 5 \cos(\omega t + 75^\circ) - 3 \cos(\omega t - 75^\circ) + 4 \sin(\omega t) &= \\ 3.763 \cos(\omega t + 82.09^\circ) \end{aligned}$$

***P5.24.** Suppose that $v_1(t) = 100 \cos(\omega t)$ and $v_2(t) = 100 \sin(\omega t)$. Use phasors to reduce the sum $v_s(t) = v_1(t) + v_2(t)$ to a single term of the form $V_m \cos(\omega t + \theta)$. Draw a phasor diagram, showing \mathbf{V}_1 , \mathbf{V}_2 , and \mathbf{V}_s . State the phase relationships between each pair of these phasors.

P5.24*

$$v_1(t) = 100 \cos(\omega t)$$


$$v_2(t) = 100 \sin(\omega t) = 100 \cos(\omega t - 90^\circ)$$

$$\mathbf{V}_1 = 100\angle 0^\circ = 100$$

$$\mathbf{V}_2 = 100\angle -90^\circ = -j100$$

$$\mathbf{V}_s = \mathbf{V}_1 + \mathbf{V}_2 = 100 - j100 = 141.4\angle -45^\circ$$
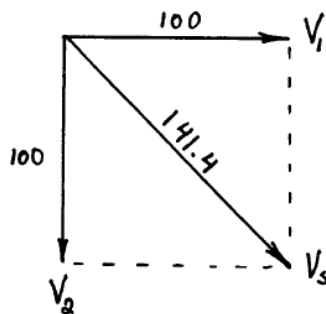
$$v_s(t) = 141.4 \cos(\omega t - 45^\circ)$$



\mathbf{V}_2 lags \mathbf{V}_1 by 90°

\mathbf{V}_s lags \mathbf{V}_1 by 45°

\mathbf{V}_s leads \mathbf{V}_2 by 45°

***P5.35.** A voltage $v_L(t) = 10 \cos(2000\pi t)$ is applied to a 100-mH inductance. Find the complex impedance of the inductance. Find the phasor voltage and current, and construct a phasor diagram. Write the current as a function of time. Sketch the voltage and current to scale versus time. State the phase relationship between the current and voltage.

P5.35*

$$v_L(t) = 10 \cos(2000\pi t)$$

$$\omega = 2000\pi$$


$$Z_L = j\omega L = j200\pi = 200\pi \angle 90^\circ$$

$$\mathbf{V}_L = 10 \angle 0^\circ$$

$$\mathbf{I}_L = \mathbf{V}_L / Z_L = (1/20\pi) \angle -90^\circ$$

$$i_L(t) = (1/20\pi) \cos(2000\pi t - 90^\circ) = (1/20\pi) \sin(2000\pi t)$$

$i_L(t)$ lags $v_L(t)$ by 90°

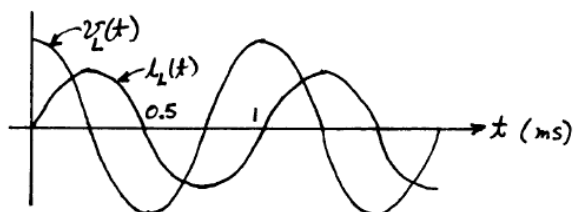

***P5.37.** A voltage $v_C(t) = 10 \cos(2000\pi t)$ is applied to a $10\text{-}\mu\text{F}$ capacitance. Find the complex impedance of the capacitance. Find the phasor voltage and current, and construct a phasor diagram. Write the current as a function of time. Sketch the voltage and current to scale versus time. State the phase relationship between the current and voltage.

P5.37*

$$v_C(t) = 10 \cos(2000\pi t)$$

$$\omega = 2000\pi$$


$$Z_C = \frac{-j}{\omega C} = -j15.92 = 15.92 \angle -90^\circ \Omega$$

$$\mathbf{V}_C = 10 \angle 0^\circ$$

$$\mathbf{I}_C = \mathbf{V}_C / Z_C = 0.6283 \angle 90^\circ$$

$$i_C(t) = 0.6283 \cos(2000\pi t + 90^\circ) = -0.6283 \sin(2000\pi t)$$

$i_C(t)$ leads $v_C(t)$ by 90°

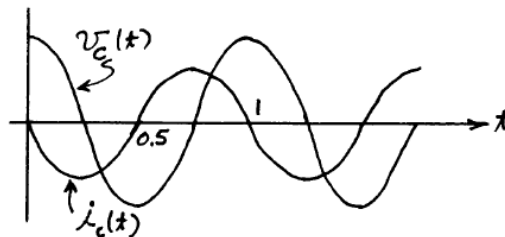

***P5.42.** Find the phasors for the current and for the voltages of the circuit shown in Figure P5.42. Construct a phasor diagram showing \mathbf{V}_s , \mathbf{I} , \mathbf{V}_R , and \mathbf{V}_L . What is the phase relationship between \mathbf{V}_s and \mathbf{I} ?


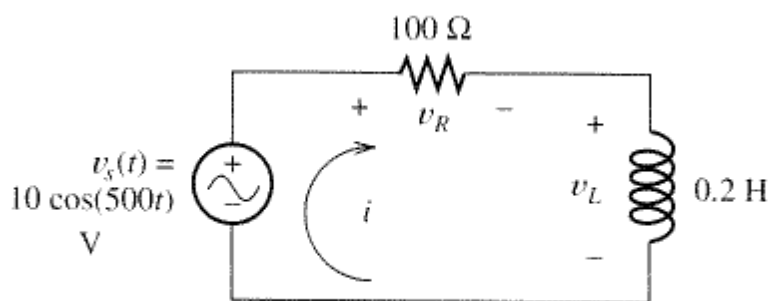


Figure P5.42

P5.42*
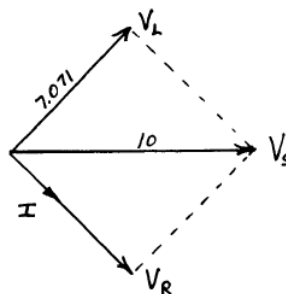
$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{R + j\omega L} \\ &= \frac{10 \angle 0^\circ}{100 + j100} \\ &= 70.71 \angle -45^\circ \text{ mA} \\ \mathbf{V}_R &= R\mathbf{I} = 7.071 \angle -45^\circ \text{ V} \\ \mathbf{V}_L &= j\omega L\mathbf{I} = 7.071 \angle 45^\circ \text{ V} \\ \mathbf{I} &\text{ lags } \mathbf{V}_s \text{ by } 45^\circ \end{aligned}$$



***P5.44.** Find the phasors for the current and the voltages for the circuit shown in Figure P5.44. Construct a phasor diagram showing \mathbf{V}_s , \mathbf{I} , \mathbf{V}_R , and \mathbf{V}_C . What is the phase relationship between \mathbf{V}_s and \mathbf{I} ?


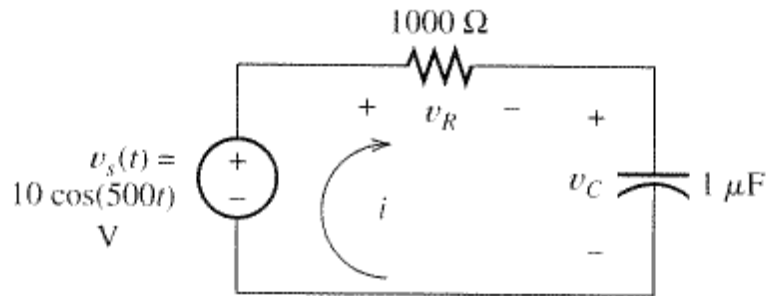


Figure P5.44

P5.44*
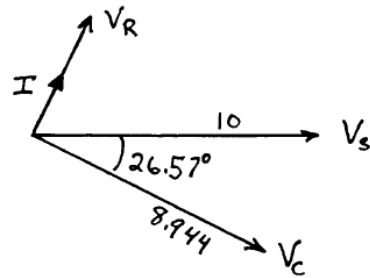
$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{R - j/\omega C} \\ &= \frac{10 \angle 0^\circ}{1000 - j2000} \\ &= 4.472 \angle 63.43^\circ \text{ mA} \\ \mathbf{V}_R &= R\mathbf{I} = 4.472 \angle 63.43^\circ \text{ V} \\ \mathbf{V}_C &= (-j/\omega C)\mathbf{I} = 8.944 \angle -26.57^\circ \text{ V} \\ \mathbf{I} &\text{ leads } \mathbf{V}_s \text{ by } 63.43^\circ \end{aligned}$$



P5.47. Compute the complex impedance of the network shown in Figure P5.47 for $\omega = 500$. Repeat for $\omega = 1000$ and $\omega = 2000$. Give the answers in both polar and rectangular forms.

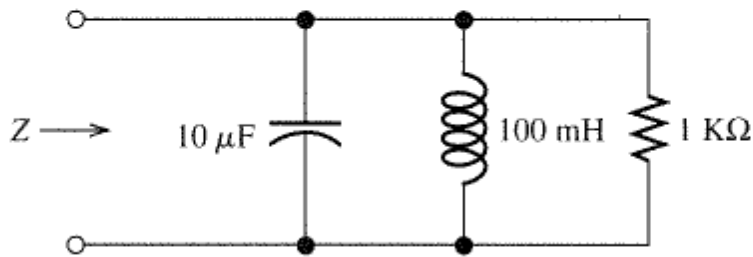


Figure P5.47

P5.47

$$Z = \frac{1}{1/Z_L + 1/Z_C} = \frac{1}{1/j\omega L + j\omega C + 1/R}$$

$$\omega = 500: \quad Z = \frac{1}{1/(j50) + j0.005 + 0.001}$$

$$= 4.425 + j66.37 = 66.52 \angle 86.19^\circ \Omega$$

$$\omega = 1000: \quad Z = 1000 + j0 = 1000 \angle 0^\circ \Omega$$

$$\omega = 2000: \quad Z = 4.425 - j66.37 = 66.52 \angle -86.19^\circ \Omega$$

***P5.49.** Consider the circuit shown in Figure P5.49. Find the phasors \mathbf{I}_s , \mathbf{V} , \mathbf{I}_R , \mathbf{I}_L , and \mathbf{I}_C . Compare the peak value of $i_L(t)$ with the peak value of $i_s(t)$. Do you find the answer surprising? Explain.

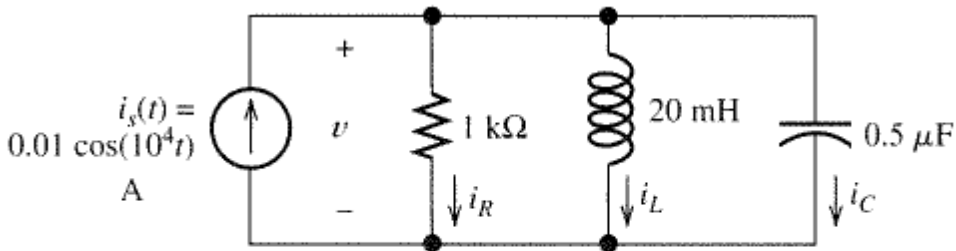


Figure P5.49

P5.49*


$$\mathbf{I}_s = 10 \angle 0^\circ \text{ mA}$$

$$\begin{aligned} \mathbf{V} &= \mathbf{I}_s \frac{1}{1/R + 1/j\omega L + j\omega C} \\ &= 10^{-2} \frac{1}{1/1000 - j0.005 + j0.005} \\ &= 10 \angle 0^\circ \text{ V} \end{aligned}$$

$$\mathbf{I}_R = \mathbf{V}/R = 10 \angle 0^\circ \text{ mA}$$

$$\mathbf{I}_L = \mathbf{V}/j\omega L = 50 \angle -90^\circ \text{ mA}$$
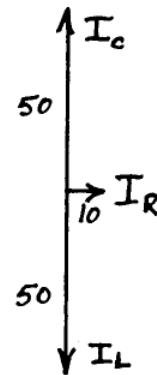
$$\mathbf{I}_C = \mathbf{V}(j\omega C) = 50 \angle 90^\circ \text{ mA}$$



The peak value of $i_L(t)$ is five times larger than the source current! This is possible because current in the capacitance balances the current in the inductance (i.e., $\mathbf{I}_L + \mathbf{I}_C = 0$).

P5.57. Solve for the node voltage shown in Figure P5.57.

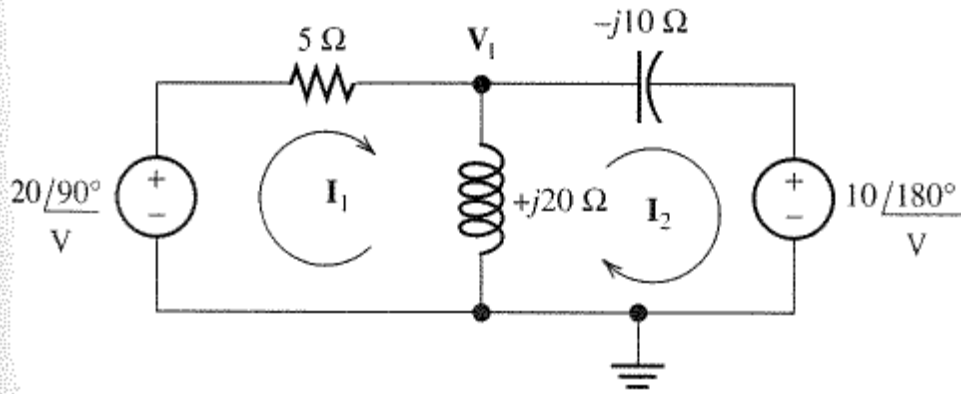


Figure P5.57

P5.57 The KCL equation is $\frac{V_1 - j20}{5} + \frac{V_1}{j20} + \frac{V_1 + 10}{-j10} = 0$. Solving, we find $V_1 = -12 + j16 = 20\angle 126.89^\circ$ V.